



filter freq. selecting circuit

Active filter
Passive filter

Active component

(L, C, R, capacitor)


V_{out}

Passive component

$\{L, C, R\}$

$V_{out} (V_{in})$
gig loss.


low pass filter → high pass filter

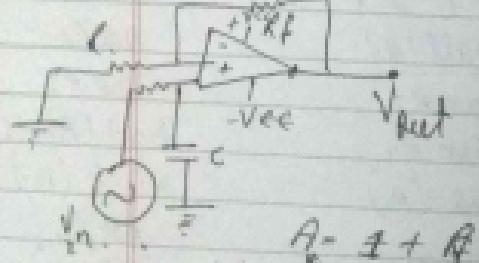


$$Z = \frac{R}{L + j\omega}$$

Low pass
1st order low pass
Resonance frequency
 $\omega_0 = \frac{1}{\sqrt{LC}}$ active filter


o - fc

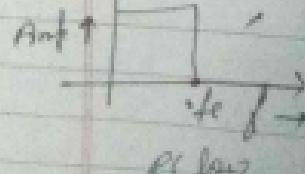

R low

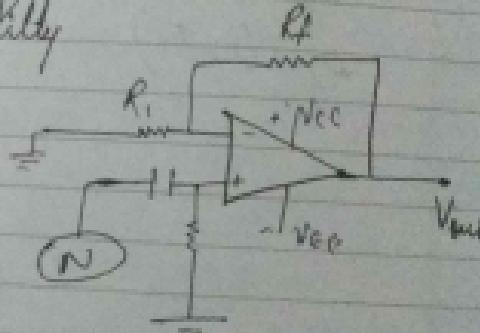


1st order high pass
filter

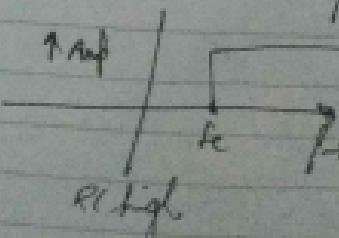

R high

RC low pass filter.

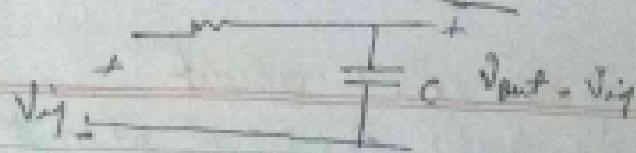

$$V_{in} \rightarrow + - \frac{1}{C} \text{ V}_{out} = V_{in}$$

$$\cdot V_{out} = \frac{1}{R+C} \omega V_{in}$$

$$|V_{out}| = \frac{1}{\omega C} f_C \cdot \frac{1}{2\pi R C}$$


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\frac{1}{\omega C})^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{\omega C}}$$

$$\frac{1}{2} = \frac{(\omega C)^2}{1 + (\frac{1}{\omega C})^2}$$

$$\omega = \frac{1}{RC}$$

RC high pass filter.

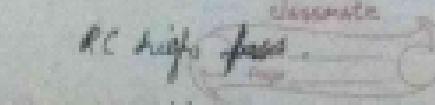


$$V_{in} \rightarrow + - \frac{1}{C} \text{ } \xi \rho \text{ V}_{out}$$

$$|V_{out}| = \frac{1}{\omega C}$$

$$|V_{out}| = \frac{R}{R + \omega C} \cdot |V_{in}|$$

$$\omega = 0 \Rightarrow |V_{out}| = 0$$

$$\omega = \infty \Rightarrow |V_{out}| = |V_{in}|$$

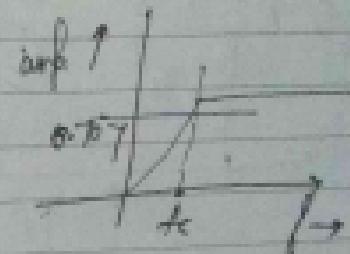

$$f_C \cdot \frac{1}{2\pi R C}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\frac{1}{\omega C})^2}}$$

$$\frac{1}{2} = \frac{1}{1 + (\frac{1}{\omega C})^2}$$


$$1 + (\frac{1}{\omega C})^2 = \frac{1}{2}$$

$$\omega C = \frac{1}{\sqrt{2}}$$

$$f_C = \frac{1}{2\pi R C}$$

Condition of resonance in series R-L-C circuit

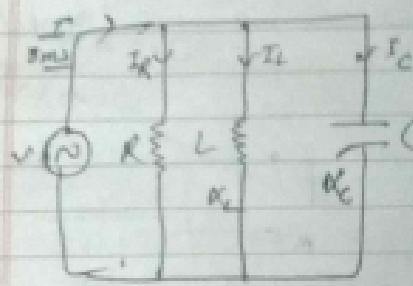
resonance occurs in a parallel R-L-C circuit when the total circuit current is "in-phase" with the supply voltage & the two reactive component cancel each other out. At resonance the admittance of the circuit is at its minimum and is equal to the conductance of the circuit.



$$V_L = V_C$$

Inductive Reactance = Capacitive reactance

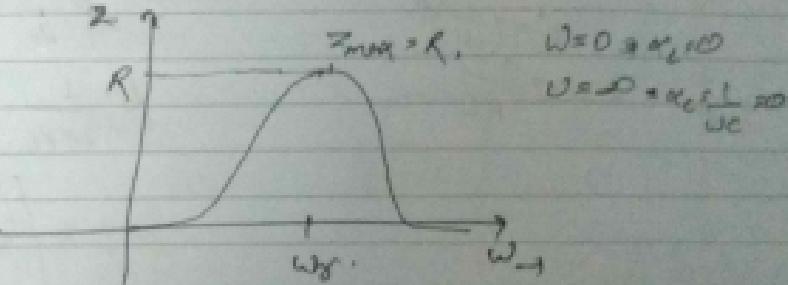voltage and current are in phase.
Impedance is zero.
Current is maximum,



current & freq:

$$I = I_R + I_L + I_C$$

$$= \frac{V}{R} + \frac{V}{j\omega L} + \frac{V}{j\omega C}$$


$$= V \left[\frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right]$$

$$= V \left[\frac{1}{R} + j \left(\omega C - \frac{1}{\omega L} \right) \right]$$

= γ admittance. (inverse of impedance)


$$\boxed{I = V \cdot \gamma}$$

mag.

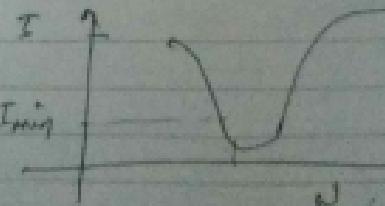

for get the monetary value of your use surely
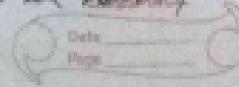
$$\omega_c = \frac{1}{LC} \quad \gamma = \frac{1}{R}$$



$$T = \frac{V}{R}$$

$\Sigma = \emptyset$ Tafedene if max -.

$$v^{\perp} = \frac{1}{\sqrt{c}}$$

$$U = \frac{I}{\sqrt{L}}$$

Arrest last half.

$$(3) \quad \text{If } f_1 = \frac{1}{\sqrt{1-x^2}}, \quad \text{then } f_2 = \frac{1}{\sqrt{1-(1-x)^2}} = \frac{1}{\sqrt{x^2}} = \frac{1}{|x|}.$$

for low freq. in circuit, will, below as a short
circuit and the current will flow through the
inductance at $\omega = 0$, so


and why $\omega = \omega \Rightarrow \omega_c = 0$

for high for. quality factory



Civet body with



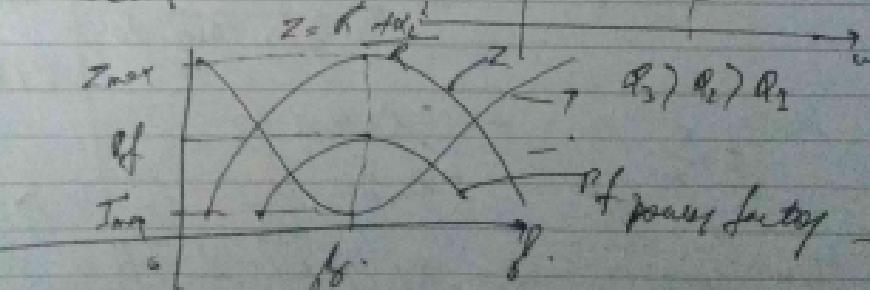power factor ($\cos\phi$) = 1) I_{mg}
resisting



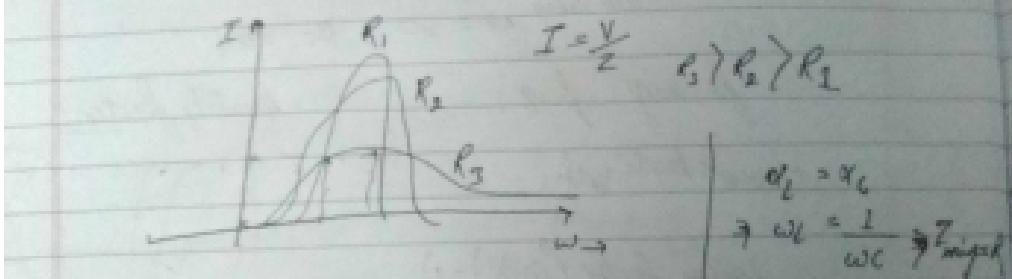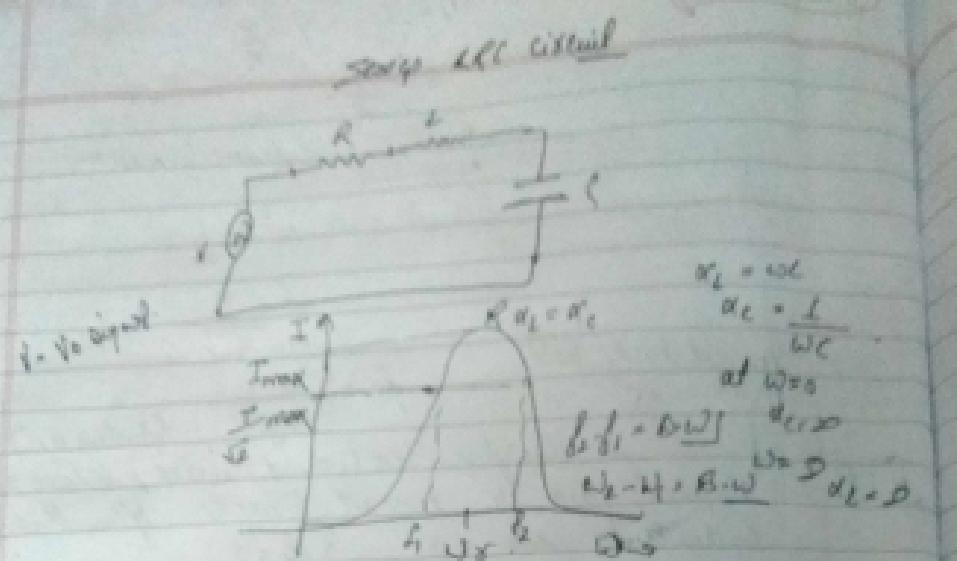freq response curve of a general, recursive circuit shows system magnitude of the current is a function of freq. at plotting this onto a graph, show us that we reverse start at its max value.



$I_{\text{max}} = \frac{V}{Z_{\text{parallel}}}$

$Z = R + j\omega L - j\frac{1}{\omega C}$

$Z = R + j\left[\omega L - \frac{1}{\omega C}\right]$

$\omega L - \frac{1}{\omega C} = 0 \Rightarrow Z_{\text{parallel}} = R$

$\omega_0 = \frac{1}{\sqrt{LC}}$

$\omega_0 = \frac{1}{\sqrt{LC}}$

$Q = \frac{I_{\text{max}}}{I_{\text{avg}}} = \frac{\omega_0}{R} = \frac{\omega_0}{R} = \frac{f}{\omega_0}$

$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

$Q = \frac{\omega_0}{\omega_0 - \omega}$

* Laplace transform of unit step function

unit step func.

$$f(t) \text{ of } u(t) = \int_0^t e^{-st} f(t) dt$$

$$\mathcal{L}\{f(t)\} = \int_0^\infty e^{-st} f(t) dt$$

$$\mathcal{L}\{u(t)\} = \int_0^\infty e^{-st} u(t) dt$$

$$\mathcal{L}\{u(t)\} = \int_{-s}^0 e^{-st} dt + \frac{1}{s} \int_0^{-s} e^{-st} dt = \frac{1}{s}$$

unit impulse function

$$u(t-a) = u(t-a) = \int_a^\infty e^{-st} dt$$

$$u(t) = \int_0^t u(t-s) ds$$

impulse function

$$\mathcal{L}\{u(t-a)\} = \int_a^\infty e^{-st} u(t-a) dt$$

$$= \int_a^\infty e^{-st} u(t-a) dt + \int_a^\infty e^{-st} u(t-a) dt$$

$$= \int_a^\infty e^{-st} dt = -\frac{1}{s} (e^{-sa})$$

$$\mathcal{L}\{u(t)\} = \int_0^\infty e^{-st} u(t) dt + \int_a^\infty e^{-st} u(t-a) dt + \int_a^\infty e^{-st} u(t-a) dt$$

$$\Rightarrow \int_a^\infty e^{-st} u(t) dt = \frac{e^{-sa}}{-s} \left[\int_a^\infty e^{-st} dt - e^{-sa} \right] = \frac{1}{s}$$

Laplace Transform of any funcy. $f(t)$ if time domain is -

$$L[f(t)] = \int_0^\infty f(t) e^{-st} dt.$$

$$= F(s) \quad \text{why } s = \sigma + j\omega$$

The function is said to be Laplace transform with $\tilde{f}(s)$

$$e^{st} dt \subset$$

freq transform is if time domain $\sigma + j\omega$ to freq domain for analysis.

inverse of this is -

$$L^{-1}[f(s)] = f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} f(s-j\omega) e^{st} ds.$$

$$\begin{aligned} L[e^{-at} f(t)] &= \int_0^\infty e^{-at} f(t) e^{-st} dt \\ &= \int_0^\infty f(t) e^{-(s+a)} dt \end{aligned}$$

$$= f(sta)$$

Convolution theory: This theory state that the convolution of two real functions is equal to the multiplication of their respective functions.

$$if L[f_1(t)] = F_1(s) \quad \& \quad L[f_2(t)] = F_2(s)$$

using Convolution it can be written as:

$$L[f_1(t) * f_2(t)] = F_1(s) * F_2(s)$$

$$\text{ie. } F(s) * L[f_1(t) * f_2(t)]$$

$$\cdot \int_0^\infty \left[\int_0^t f_1(t-y) f_2(y) dy \right] e^{-st} dt$$

$$\cdot \int_0^\infty \left[\int_0^t f_1(t-y) f_2(y) u(t-y) e^{-sy} dy \right] dt.$$

since $u(t-\gamma) = 0$ for all $t < \gamma$, the inverse integral if multiplied by $u(t-\gamma)$ is upper limit of inverse integral become \int_0^∞

$$\begin{aligned} f(s) &= \int_0^\infty f_s(\gamma) \left[\int_0^\infty u(t-\gamma) u(t-\gamma) e^{-st} dt \right] d\gamma \\ &= \int_0^\infty f_s(\gamma) e^{-st} f_s(s) d\gamma \\ &= f_s(s) \int_0^\infty f_s(\gamma) e^{-st} d\gamma = f_s(s) \cdot f_s(s). \end{aligned}$$

$$f_s(f_s(s) e^{-st} ds) = f_s(s)$$

$$L(f_s(s) e^{-st} ds) = f_s(s)$$

$$\begin{aligned} L(\sin \omega t) &\rightarrow L\left[\frac{e^{j\omega t} - e^{-j\omega t}}{2j}\right] \\ &= \frac{1}{2j} \left[\int_0^\infty e^{j\omega t} e^{-st} dt - \int_0^\infty e^{-j\omega t} e^{-st} dt \right] \\ &\rightarrow \frac{j}{2j} \left[\int_0^\infty e^{-(s-j\omega)t} dt - \int_0^\infty e^{-(s+j\omega)t} dt \right] \\ &\cdot \frac{1}{2j} \left[\frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right] = \frac{\omega}{s^2 + \omega^2} \end{aligned}$$

$$L(\sin \omega t) = L\left[\frac{e^{j\omega t} + e^{-j\omega t}}{2j}\right]$$

$$- \int_0^\infty \left(\frac{e^{j\omega t} + e^{-j\omega t}}{2j} \right) e^{-st} dt.$$

$$= \frac{1}{2} \left[\int_0^\infty e^{j\omega t} e^{-st} dt + \int_0^\infty e^{-j\omega t} e^{-st} dt \right]$$

$$= \frac{1}{2} \left[\int_0^\infty e^{-(s-j\omega)t} dt + \int_0^\infty e^{-(s+j\omega)t} dt \right]$$

$$= \frac{1}{2} \left[\frac{1}{s-j\omega} + \frac{1}{s+j\omega} \right] = \frac{1}{2} \frac{2s}{s^2 + \omega^2} = \frac{s}{s^2 + \omega^2}$$


Ramp function: $f(t) = t$ for unit ramp.

$$L[f(t)] = \int_0^\infty t e^{-st} dt$$

Integrating by parts, $= uv - \int v du$. where,
 $u = t, dv = e^{-st} dt, \frac{du}{dt} = 1, u = \frac{e^{-st}}{-s}$

$$= t \cdot \frac{e^{-st}}{-s} \Big|_0^\infty - \int_0^\infty \frac{e^{-st}}{-s} \cdot 1 \cdot dt$$

$$= \frac{1}{s^2}$$

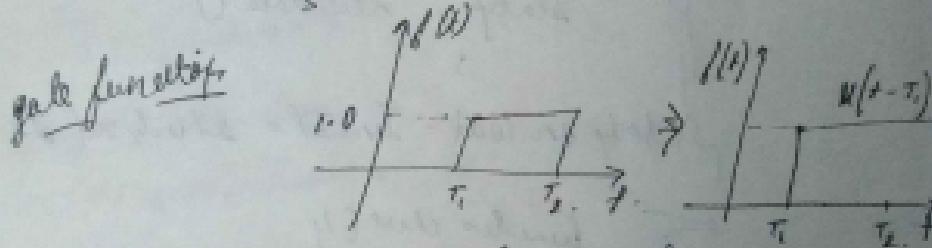


say by the laplace transfer method

$$L[f(t)] = \int_0^\infty f(t) e^{-st} dt$$

Now, we have,

$$\begin{aligned} & L[u(t-\tau_1) - u(t-\tau_2)] \\ &= L[u(t-\tau_1)] - L[u(t-\tau_2)] \\ &= \int_0^\infty u(t-\tau_1) e^{-st} dt - \int_0^\infty u(t-\tau_2) e^{-st} dt \\ &= \frac{e^{-s\tau_1}}{s} - \frac{e^{-s\tau_2}}{s} \end{aligned}$$

②

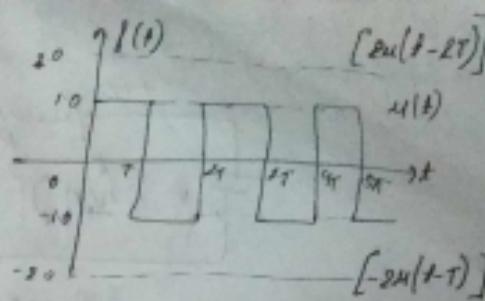

according to before we will have,

$$f(t) = u(t) - 2u(t-T) + 2u(t-2T) + \dots$$

$$\Rightarrow L(f(t)) = \frac{1}{s} \int_0^s u(t) e^{-st} dt - 2u(t-T) + 2u(t-2T) + \dots$$


$$= \int_0^s e^{-st} dt - 2u(t-T) + \dots$$

$$= \frac{1}{s} [e^{-st}]_0^s$$

$$= \frac{1}{s} \left[-2e^{-Ts} + 2e^{-2Ts} + \dots \right]$$

$$= \frac{1}{s} \left[1 - 2e^{-Ts} \left(1 - e^{-Ts} + e^{-2Ts} - e^{-3Ts} + \dots \right) \right]$$

③

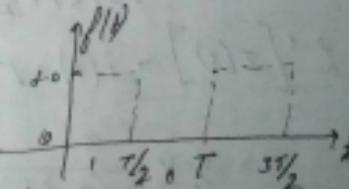


$$f(t) = 1; \quad 0 \leq t < T/2$$


$$= 0; \quad T/2 \leq t < T$$

$$L(f(t)) = \left(\frac{1}{1-e^{-sT}} \right) \left[\int_0^{T/2} 1 \cdot e^{-st} dt + \int_{T/2}^T 0 \cdot e^{-st} dt \right]$$
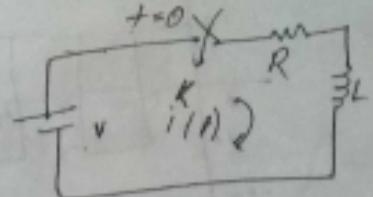
$$= \frac{1}{s} \frac{(1-e^{-sT/2})}{(1-e^{-sT})}$$


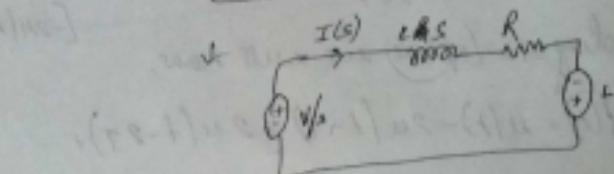
$$\begin{aligned} I &= \frac{V}{R} \\ V &= IR \\ I &= \frac{V}{R} = \frac{V}{3} \end{aligned}$$



$\xrightarrow{\text{KVL}}$

$$L \frac{di(t)}{dt} + R i(t) = V$$

Taking Laplace transform

$$L [sI(s) - i(0)] + RI(s) = V/s$$

Now, $i(0) = 0$ as the initial current through inductor
is zero.

$$\text{so, } I(s) = \frac{V}{Ls(s+R/L)}$$

$$I^{-1}[I(s)] = i(t) = L^{-1}\left[\frac{A}{s} + \frac{B}{s+R/L}\right]$$

where,

$$A = \frac{V}{L} \Big|_{s=0} = \frac{V}{R}$$


$$B = \frac{V}{L} \frac{(s+R/L)}{s(s+R/L)} \Big|_{s=-R/L} = -V/R$$

$$i(t) = \frac{V}{R} L^{-1}\left[\frac{1}{s} - \frac{1}{s+R/L}\right] = \frac{V}{R} [1 - e^{-t/(R/L)}]$$


at. $t=0$; $i(t)=0$

$$t=\infty; i(t)=V/R$$
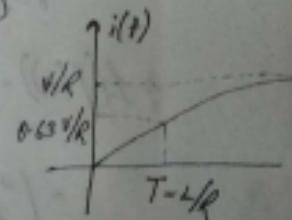
$$t=V/R; i(t)=V/R (1-e^{-1}) = 0.63 V/R$$



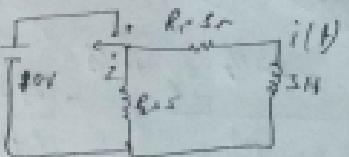$T = t/R$ if known \Rightarrow time constant of circuit & is defined w.r.t. the interval after which current rises to 63% of steady state value.



Let us determine the steady state condition just before the switch is moved to position 2.

$$i.e. i(0-) = \frac{V_0}{R_1 + R_2} = i_L(0+)$$

when the switch is in position 2 by t_{switch} :

$$\Rightarrow L \frac{di}{dt} + (R_1 + R_2)i = 0$$

Now taking Laplace transform:

$$\Rightarrow [sI(s) - i_L(0+)] + (R_1 + R_2) I(s) = 0$$

$$R_1 + R_2 = 3\Omega, R_1 = R_2 = 1.5\Omega$$

$$I(s)(3s + 10) = 4i_L(0+) = 3,$$

$$I(s) = \frac{3}{3s + 10} = \frac{3}{3s + 3 + 7} = \frac{3}{s + 1 + \frac{7}{3}}$$

$$\Rightarrow i(t) = L^{-1}(I(s)) = L^{-1}\left(\frac{3}{s + 1 + \frac{7}{3}}\right) = 3e^{-\frac{10}{3}t}$$

$$f(t) = \begin{cases} 0 & t < -T_2 \\ 1 & -T_2 \leq t \leq T_2 \\ 0 & t > T_2 \end{cases}$$



$$f(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_{-\infty}^{-T_2} 0 e^{-j\omega t} dt + \int_{-T_2}^{T_2} 1 e^{-j\omega t} dt + \int_{T_2}^{\infty} 0 e^{-j\omega t} dt.$$

$$= \int_{-\pi/T_2}^{\pi/T_2} f(t) e^{-j\omega t} dt = \left[\frac{e^{-j\omega t}}{-j\omega} \right]_{-\pi/T_2}^{\pi/T_2}$$

$$= \frac{e^{j\omega \pi/T_2} - e^{-j\omega \pi/T_2}}{j\omega} = \frac{2j \sin(\omega \pi/T_2)}{j\omega}$$

Now take $\omega = \frac{2}{T} \sin(\omega \pi/T_2)$


$$f(\omega) = \frac{T \cdot \sin(\omega \pi/T_2)}{(\omega \pi/T_2)} = \frac{T \sin x}{x} = T \text{sinc}(x)$$

where, $x = \omega \pi/T_2$ & $\text{sinc}(x) = \frac{\sin x}{x}$ is called sinc function.

Now, when $x \rightarrow 0$, $\text{sinc}(x) \rightarrow 1$

$$\text{if } x = \pm n\pi, \text{sinc}(x) = 0$$
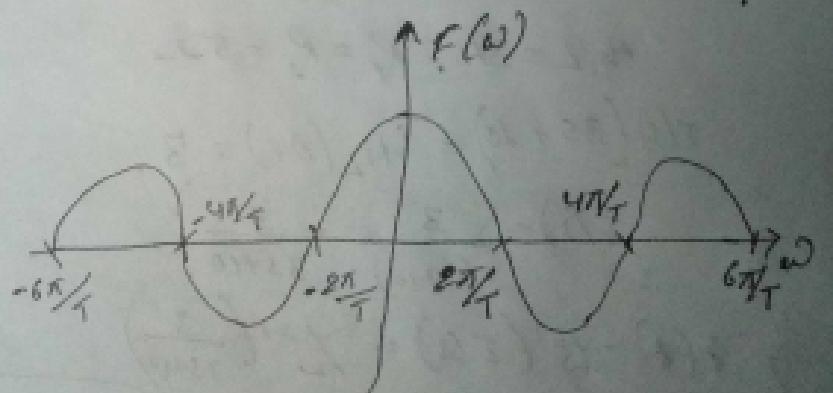
$$\therefore \omega \pi/T_2 = \pm m\pi, \omega = \pm \frac{2m\pi}{T}, m = 0, \pm 1, \pm 2, \dots$$




Q) diff between linear and non-linear network?

linear

Any network whose parameter are constant i.e. they don't change with voltage or current passing through that network.

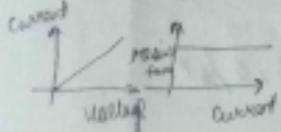
Principle of superposition is valid only in linear network.



non-linear

It is that network whose parameter are changed with voltage or current passing through it.

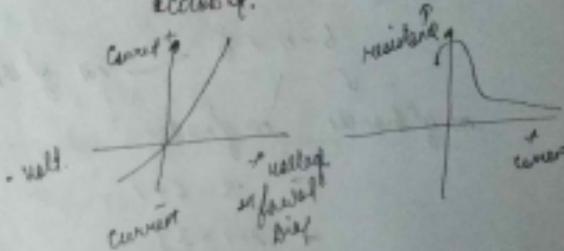Ex network having diode rectifier, say parameter of diode, i.e. diode resistance is changed with voltage across it.



diff between node & mesh

node

A terminal of any branch of a network connected to two or more branches if known as node. Voltage of any node with respect to ground the node voltage. Voltage between any pair of nodes is node pair voltage.

mesh

A set of branches forming a closed path, except the branching of any branch making the path open - but not have any other circuit inside it.

Active

A network containing energy source (voltage or current source) together with other circuit elements.

passive


A network containing circuit elements without any energy source (i.e. voltage or current source).

Lumped

A network in which physical of space Network in which resistors, capacitors & inductors can be represented.

distributed

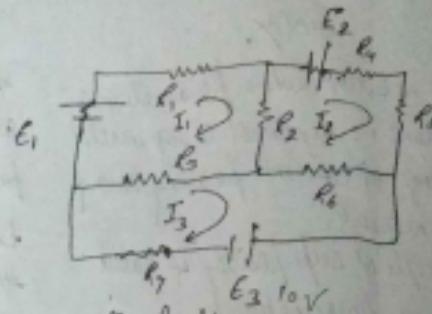Resistor, capacitor & inductor cannot be electrically operated individually isolated as separate elements.
Ex: Transmitting network.



no. of loop eqⁿ to be solved!

$$\begin{aligned} b - n + s &= \text{no. of nodes} \\ \text{no. of branches} &\quad \text{no. of nodes} \\ &= 8 - 6 + 1 \\ &= 3 \end{aligned}$$

In loop ①

$$I_1 R_1 + (I_1 - I_2) R_2 + (I_1 - I_3) R_3 - E_1 = 0$$

$$\Rightarrow I_1 (R_1 + R_2 + R_3) - I_2 R_2 - I_3 R_3 = E_1 = 0$$

In loop ②

$$-E_2 + I_2 R_4 + I_2 R_5 + (I_2 - I_3) R_6 + (I_2 - I_1) R_7 = 0$$


$$\Rightarrow I_2 (R_4 + R_5 + R_6 + R_7) - I_1 R_2 - I_3 R_6 = E_2 = 0 \quad \text{---(2)}$$

In loop ③

$$(I_3 - I_1) R_1 + (I_3 - I_2) R_6 + E_3 = 0 + I_3 R_7 = 0$$

$$\Rightarrow I_3 (R_1 + R_6 + R_7) - I_1 R_3 - I_2 R_6 = -E_3 = 0 \quad \text{---(3)}$$
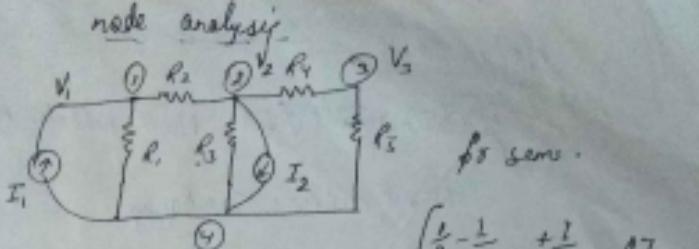
$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_2 & -R_3 \\ -R_2 & (R_4 + R_5 + R_6 + R_7) & -R_6 \\ -R_3 & -R_6 & (R_1 + R_6 + R_7) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ -E_3 \end{bmatrix}$$



for sens.

$$\begin{array}{l} \text{if } (n-1) > (b-n+r) \\ \quad \rightarrow \text{loop analysis is preferred} \end{array}$$

$$\begin{array}{l} \text{if } (n-1) < (b-n+r) \\ \quad \rightarrow \text{node analysis is preferred} \end{array}$$

if node - I using (xcii):

$$I_1 - V_1/R_1 - (V_1 - V_2)/R_2 = 0$$

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - V_2 \cdot \frac{1}{R_2} = I_1 - (i)$$

At node - II:

$$-I_2 - V_2/R_3 - \underbrace{(V_2 - V_1)}_{R_2} + \frac{V_1 - V_3}{R_4} = 0$$


$$\therefore I_2 = V_2 \left(\frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} \right) - \frac{V_1}{R_2} + \frac{V_3}{R_4} - (ii)$$

At node - III:


$$-\frac{V_3}{R_5} = 0 + \frac{(V_2 - V_3)}{R_4}$$

$$V_2 \left(\frac{1}{R_5} + \frac{1}{R_4} \right) - \frac{V_3}{R_4} = (iii)$$
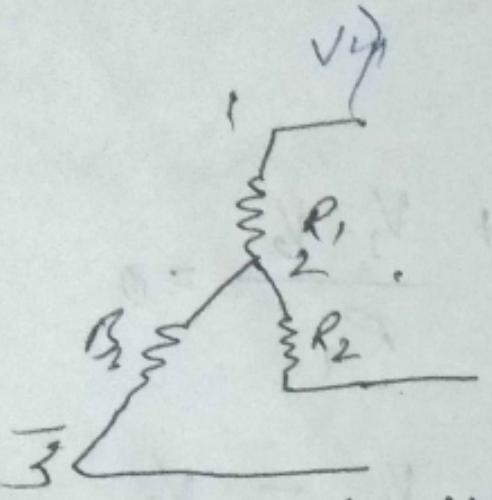
$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_4} & -\frac{1}{R_4} \\ 0 & -\frac{1}{R_4} & \frac{1}{R_5} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ -I_2 \\ 0 \end{bmatrix}$$



Symmetry.

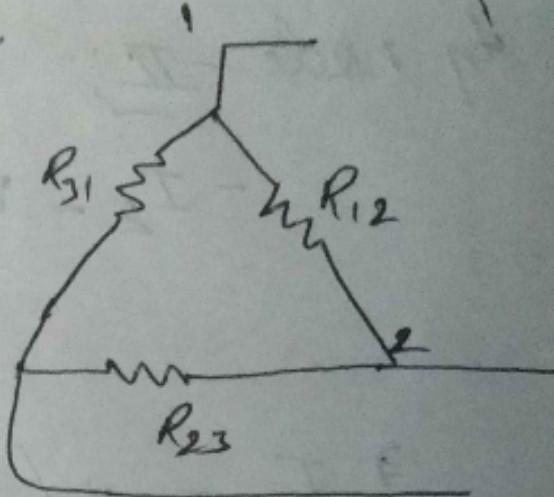

eq = delta network.

resist behv ① ④

$$R_{1\text{all}} (R_{23} + R_{31})$$

$$\frac{R_1 \times (R_2 + R_3)}{R_1 + R_2 + R_3}$$

$$= R_{12} + \cancel{R_{23}} \quad \text{①}$$

$$\textcircled{②} \quad R_2 \text{all} (R_3 + R_1)$$

$$R_{23} - \textcircled{④} \quad R_{31} - \textcircled{④}$$


$$R_{12} \times R_{23} = \frac{R_1 \times (R_2 + R_3)}{R_1 + R_2 + R_3} \cdot \frac{R_2 (R_3 + R_1)}{R_1 + R_3}$$

$$\left. \begin{array}{l} R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} \\ R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} \\ R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2} \end{array} \right\}$$


$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

delta / star conversion

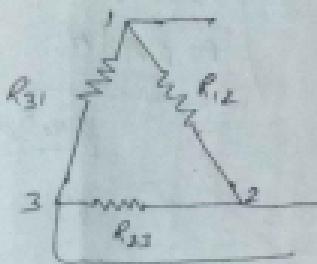

delta network

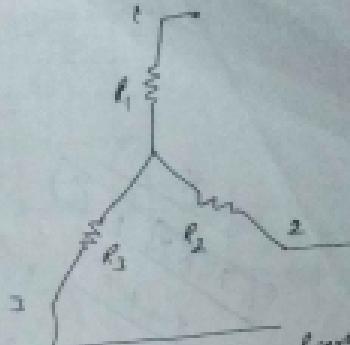

equi star network

$$\text{resistance between node } \odot \text{ & } \odot: R_{12} // (R_{23} + R_{31})$$

$$= \frac{R_{12} \times (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

- equivalent resistance between
node 1 & 2 in star network.
 $\approx R_1 + R_2$ -- (i)

$$\text{resistance between node } \odot \text{ & } \odot: \frac{R_{23} // (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}}$$

$\approx R_2 + R_3 - \odot$

similarly,

$$\frac{R_{31} \times (R_{23} + R_{12})}{R_{12} + R_{23} + R_{31}} = R_1 + R_3 - \odot$$

sub eq (i) from (j) and adding result to eq (i), we get;

$$R_1 + R_3 - R_1 \approx R_2 \\ 2R_3 = \frac{2R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$


$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{31}} \quad R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

~~3~~ ~~4~~

* Circuit will resonate when reactance or inductance
opposite of current is zero. Frequency is called.
resonant freq (f_r)

Thévenin's theorem! Norton's theorem!

Any two terminal linear, bilateral, active network containing energy source (voltage or current source) & impedance can be replaced with an equivalent circuit consisting of a voltage source ϵ' in series with an impedance z' . The value of ϵ' is the open circuit voltage between the terminals of the network & z' is the input measured between the terminals of network with all energy sources eliminated (but not the internal impedance if any).

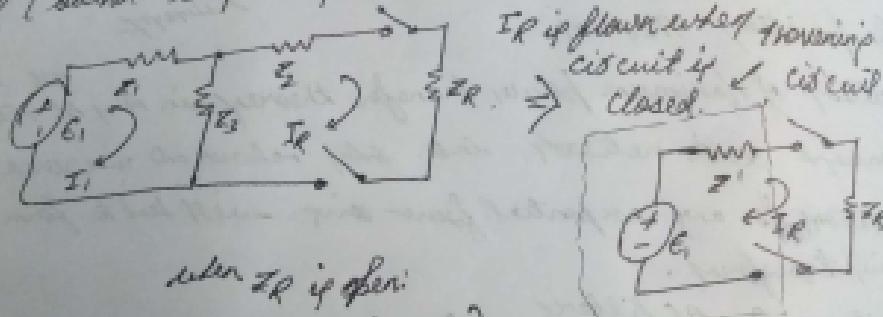

when Z_R is open:

$$E_1 = I_1(Z_1 + Z_2)$$

$$I_1 = E_1 / (Z_1 + Z_2)$$

at open circuit of Z_R terminals no I_R is flowing so,
no voltage drop in Z_R ($: Z_R I_R = 0$)

$$\text{So, open circuit voltage } = E_1 = Z_2 I_1 = \frac{E_1 Z_2}{Z_1 + Z_2}$$

Thévenin's Equivalent is

$$Z' = \left(Z_1 / (Z_1 + Z_2) \right) + Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2} + Z_2$$

$$= \frac{Z_1 + Z_2 + Z_1 Z_2 + Z_1 Z_2}{Z_1 + Z_2}$$


say current passing through

$$Z_R = \frac{e_1}{(Z_1 + Z_R)} = \left(\frac{6, Z_3}{Z_1 + Z_3} \right)$$


$$\left\{ \left(\frac{(Z_1 Z_3 + Z_2, Z_2 + Z_3 Z_1)}{Z_1 + Z_3} \right) + Z_R \right\}$$

Noon's

Any two terminal line, active, bilateral network containing energy source (voltage or current source) can be replaced by an equivalent circuit consisting of a current source I' in parallel with an admittance y' . The value of I' is the short circuit current between the terminals of the network & y' is the admittance measured between the terminals with all energy source eliminated (but not their internal admittance in any).

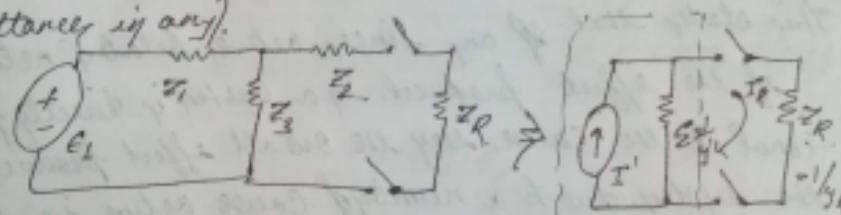

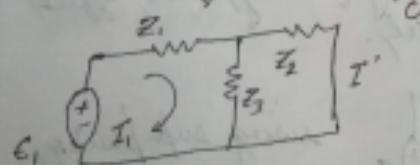\Downarrow I_R is flows when closed circuit Noon's



At loop - I'

$$e_1 - I_z z_1 + (I_z - I') z_3 = 0$$

$$I_z (z_1 + z_3) - I' z_3 = e_1 \quad (i)$$

at loop - II'

$$z_2 I' + (I' - I_z) z_3 = 0$$

$$I_z z_3 = I' (z_2 + z_3)$$

$$I_z = I' (z_2 + z_3) / z_3 \quad (ii)$$

putting (i) in (ii) at the value of I_z , we get

$$I' = e_1 / \left\{ \left(1 + \frac{z_2}{z_3} \right) \left(1 + \frac{z_1}{z_3} \right) - z_3 \right\}$$

Noorbi's equivalent admittance $\gamma' =$

$$\text{where } z' = (z_1 // z_3) + z_2$$

$$= \frac{z_1 z_3}{z_1 + z_3} + z_2$$


$$= \frac{(z_1 z_3 + z_1 z_2 + z_3 z_2)}{z_1 + z_3},$$

So,

$$I_R = \left(\frac{z'}{z' + z_R} \right) \cdot I'$$

Superposition theory

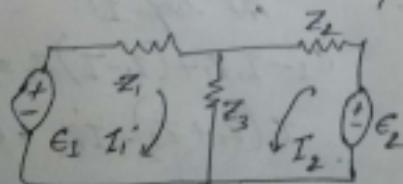
This states that if any linear, active, bilateral network, if the effect produced in a system is directly proportional to the cause, then the overall effect produced in the system, due to a number of cause acting jointly, can be determined by superposing (adding) the effects of each source across separately.



using superposition,

consider E_1 source only.


① \downarrow but E_2 is replaceable

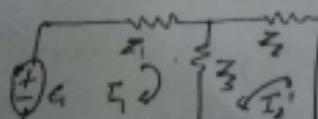

internal impedance of any

similarly, using the theory considering only ϵ_2 source but ϵ_1 is replaced by its internal impedance if

only -

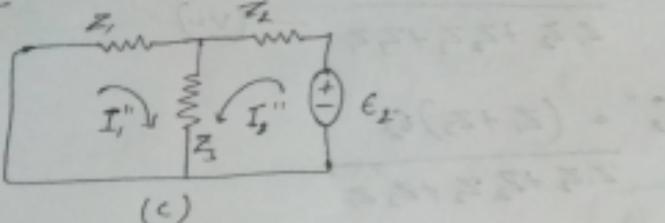

$$\text{from fig (a)} \quad \epsilon_1 = I_1(Z_1 + Z_3) + I_2 Z_3 \quad \text{--- (i)}$$

$$\epsilon_2 = I_1 Z_3 + I_2 (Z_2 + Z_3) \quad \text{--- (ii)}$$

solving /

$$I_1 = \frac{(Z_2 + Z_3) \epsilon_1}{(Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1)} - \frac{Z_3 \epsilon_2}{(Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1)} \quad \text{--- (iii)}$$

$$I_2 = \frac{-Z_3 \epsilon_1}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} + \frac{(Z_1 + Z_2) \epsilon_2}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} \quad \text{--- (iv)}$$

$$\text{from fig (b)} \quad \epsilon_1 = I_1'(Z_1 + Z_3) + I_2' Z_3$$

$$\theta = I_1' Z_3 + I_2' (Z_2 + Z_3)$$

solving, $I_1' = \left[\frac{Z_2 + Z_3}{Z_1 Z_3 + Z_2 Z_3 + Z_3 Z_1} \right] \epsilon_1 \quad \text{--- (v)}$

$$I_2' = \frac{-Z_3 \cdot \epsilon_1}{Z_1 Z_3 + Z_2 Z_3 + Z_3 Z_1} \quad \text{--- (vi)}$$

from fig (c):

$$0 = I_1''(Z_1 + Z_3) + I_2''' Z_3$$

$$\epsilon_2 = I_1'' Z_3 + I_2'' (Z_3 + Z_2)$$

solving

$$I_1' = \frac{-Z_3 E_2}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} - (v)$$


$$I_2'' = \frac{(Z_1 + Z_2) E_2}{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}$$

Note. $I_1 = I_1' + I_2''$ as in eq (18)

$I_2 = I_2' + I_2''$ as in eq (19)

maximum power - formula

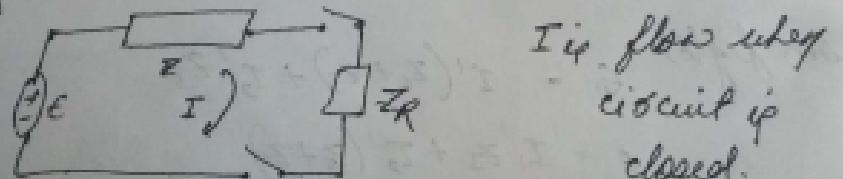maximum power will be delivered by a network when
impedance Z_L if the impedance of Z_L is the complex
conjugate of the impedance of Z of the network measured
looking back into the terminals of the network.



Say, $Z = R + jX$, $Z_L = R_L + jX_L$.

$$V = IR \quad I = \frac{e}{Z + Z_L} = \frac{e}{(R + R_L) + j(X + X_L)}$$

power delivered to load:

$$P = I^2 R_L = \frac{e^2 R_L}{(R + R_L)^2 + (X + X_L)^2}$$

for maximum power delivery

$$\left[\frac{dp}{dx_R} = 0 \right] = \frac{-2\epsilon^2 R_R (\alpha_R + \alpha)}{[(R_R + R)^2 + (\alpha_R + \alpha)^2]^2}$$

or, $\alpha_R + \alpha = 0$

$$\alpha_R^* = -\alpha$$

$$P = I^2 R_R$$

putting $\alpha_R = -\alpha$ in power delivery eqn,

$$P = \frac{\epsilon^2 R_R}{(R_R + R)^2}$$

for max \cong power

$$\left[\frac{dp}{dr_L} = 0 \right] = \frac{\epsilon^2 (R_R + R)^2 - 2\epsilon^2 R_R (R + R_L)}{(R_R + R)^4}$$

or $\epsilon^2 (R_R + R) - 2\epsilon^2 R_R = 0$ $\cancel{[(R_R + R)^2 - R_R + R_L] \epsilon^2}$

$$= R_R = R$$

So, conclusion is maximum power is delivered to any load if load impedance is complex conjugate of internal network impedance
maximum power transferred to any load is

$$P_{\max} = \frac{\epsilon^2 R_R}{(R_R + R)^2} = \frac{\epsilon^2 R_R}{(2R_R)^2} = \frac{\epsilon^2 R_R}{4R_R^2} = \frac{\epsilon^2}{4R_R} \quad \boxed{Q}$$